Mail ID: bu8486@srmist.edu.in

# **Project 1: RGB Pattern**

## Abstract:

Creating color changing of RGB led using Arduino in Tinkercad platform.

### Introduction:

A color-changing RGB led is created by passing different inputs in the potentiometer through a well-structured code using an Arduino Uno.

#### Methodology:

- Place a Arduino Uno, a breadboard, a LED RGB and three potentiometers.
- Place LED RGB on breadboard in pin number 4. Connect the LED RGB pin 4 to arduino input terminal of pin 11 through a normal wire.
- Similarly, to the pin numbers of 6 and 7 of LED RGB connect to the input terminals of arduino 10 and 9 respectively.
- To the 5 pin of LED RGB, place a resistor on the breadboard from d to f and connect from pin a to negative terminal of breadboard.
- To produce a RED color, a potentiometer is placed at pin 12. Similarly, to get GREEN and BLUE color potentiometers are placed at pin 18 and 24 respectively.
- For RED color potentiometer a wire is connected from negative terminal to f in the pin 12 on breadboard. Connect a wire from f to e and from a to **A0** in arduino. In pin 14 connect a wire from positive terminal to f.
- For BLUE color potentiometer a wire is connected from negative terminal to f of pin 18. Connect a wire from f to e and from a to **A1** in arduino. In pin 20, connect a wire from positive terminal to f.
- For GREEN color potentiometer a wire is connected from negative terminal to f of pin 24. Connect a wire from f to e and from a to **A2** in arduino. In pin 26, connect a wire from positive terminal to f.
- Connect a normal wire from **GND** of Arduino to negative terminal of breadboard and **5V** of Arduino to positive terminal of breadboard.


#### CODE:


```
const int red = 11;
const int blue = 10;
const int green = 9;
void setup(){
 pinMode(red, OUTPUT); // Red
 pinMode(blue, OUTPUT); // Blue
 pinMode(green, OUTPUT); // Green
 pinMode(A0, INPUT); // Red
 pinMode(A1, INPUT); // Blue
 pinMode(A2, INPUT); // Green
 Serial.begin(9600);
}
void loop() {
 int r_value = analogRead(A0);
 int b_value = analogRead(A1);
 int g_value = analogRead(A2);
 int m_r_value = map(r_value, 0, 1023, 0, 255); // mapping to get limited values
 int m_b_value = map(b_value, 0, 1023, 0, 255);
 int m_g_value = map(g_value, 0, 1023, 0, 255);
 analogWrite(red, m_r_value);
 analogWrite(blue, m_b_value);
 analogWrite(green, m_g_value);
 Serial.print(m_r_value);
```

```
Serial.print(" ");
 Serial.print(m_b_value);
 Serial.print(" ");
 Serial.println(m_g_value);
 Serial.print(" ");
SCREENSHOTS:
                                             <u>+</u> = A-
                                                                                                                       1 (Arduino Uno R3)
   Text
    1 const int red = 11;
    2 const int blue = 10;
    3 const int green = 9;
    5 void setup(){
         pinMode(red, OUTPUT); // Red
        primode (red, OUTPUT); // Red
pinMode (blue, OUTPUT); // Blue
pinMode (green, OUTPUT); // Green
pinMode (A0, INPUT); // Red
pinMode (A1, INPUT); // Blue
pinMode (A2, INPUT); // Green
Serial hegin(0600);
    9
         Serial.begin(9600);
  13 }
  14
  15 void loop() {
  int r_value = analogRead(A0);
int b_value = analogRead(A1);
int g_value = analogRead(A2);
        int m_r_value = map(r_value, 0, 1023, 0, 255); // mapping to get limited values
int m_b_value = map(b_value, 0, 1023, 0, 255);
int m_g_value = map(g_value, 0, 1023, 0, 255);
   21
   23
   24
        analogWrite(red, m_r_value);
        analogWrite(blue, m_b_value);
analogWrite(green, m_g_value);
   26
   28
   29
        Serial.print(m_r_value);
Serial.print("");
  32 Serial.print(m_b_value);
33 Serial.print("");
                 Serial.print(" ");
    33
                 Serial.println(m g value);
    34
    35
                 Serial.print(" ");
    36
```

```
Serial Monitor
142 0 1/8
142 0 178
142 0 178
142 0 178
142 0 178
142 0 178
142 0 178
```
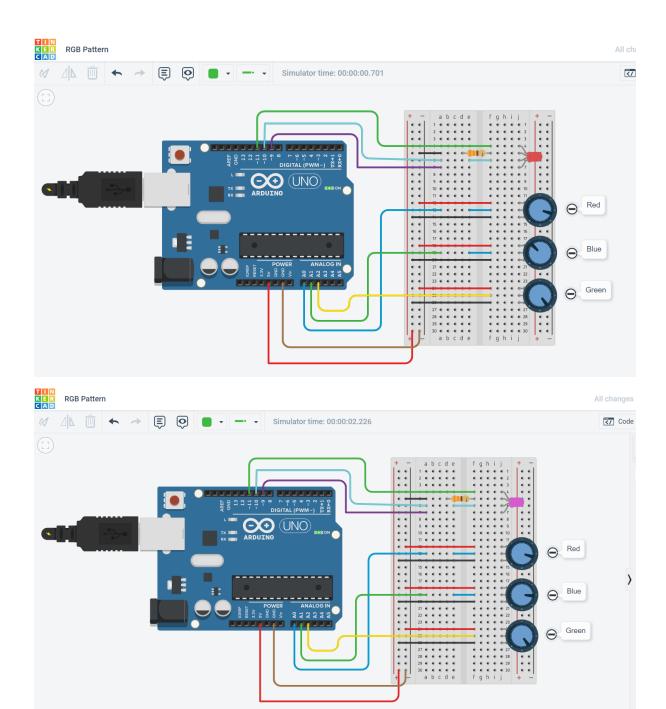
## LED COLOR CHANGING FOR DIFFERENT INPUTS:



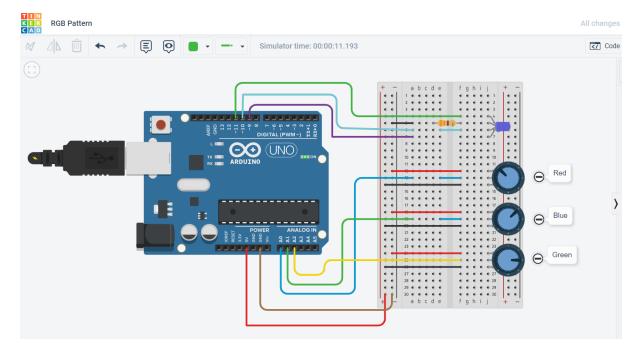

## Conclusion:

RGB LED has implemented successfully with well-structured code and with proper connections of components.